





# EEL1010 Introduction to Electrical Engineering

## Lab Report


Name	Lokesh Tanwar
Roll Number	B21EE035
Experiment No	03
Experiment Title	Verification of KVL in RL and RC AC Circuits

**Objective:-** To verify KVL and find power factor in R-L and R-C series AC circuits.


**Circuit Diagram:-**

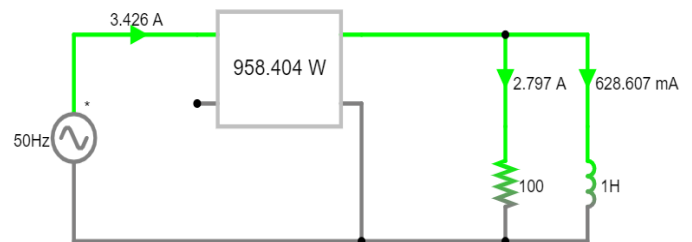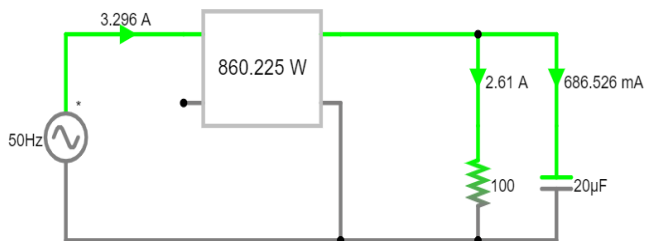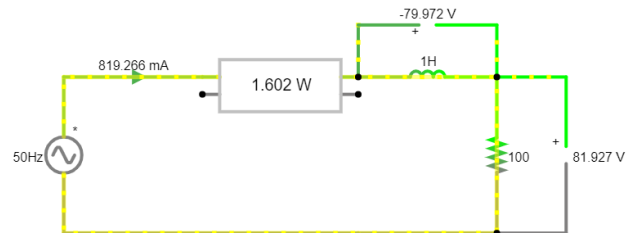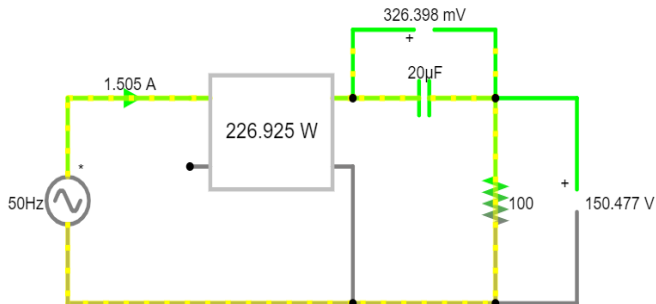


# Experiment 1(R-L Series Circuit) Falstad simulation readings

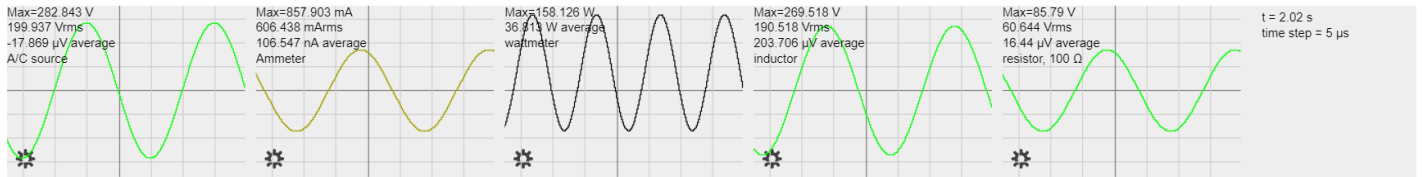

At 200V

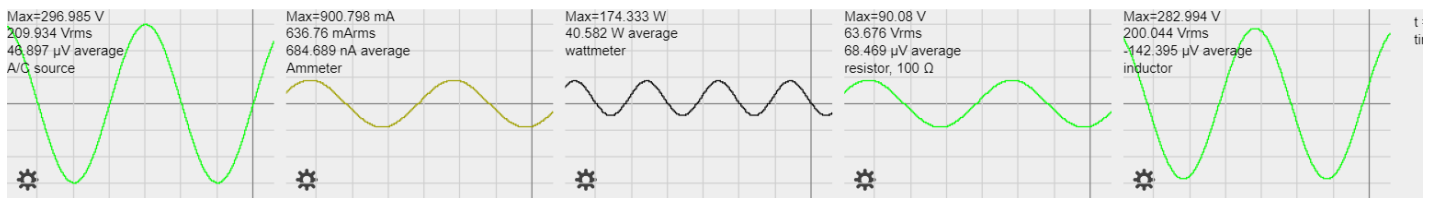

At 210V

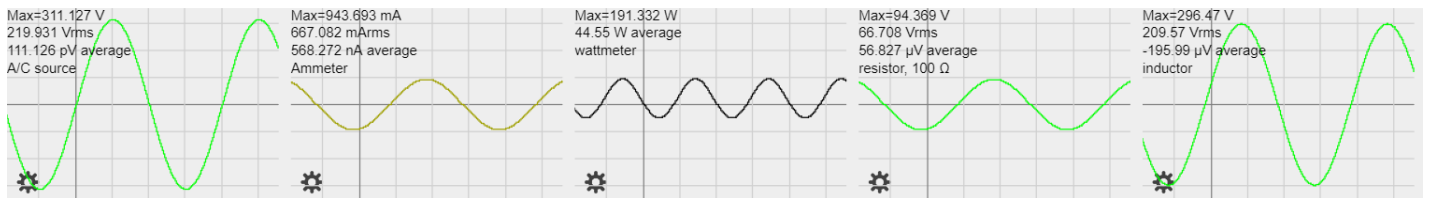


At 220V


**Calculations:-**

S. No.	Variac V <sub>s</sub>	V <sub>L</sub>	V <sub>R</sub>	I	W	Calculated $V=\sqrt{V_L^2 + V_R^2}$	Power factor (Measured) $\cos\phi = \frac{W}{(V_s I)}$	Power factor (Measured 2) $\cos\phi = \cos[\tan^{-1}(\frac{V_L}{V_R})]$	Power factor (Measured 3) $\cos\phi = \frac{V^2+V_R^2-V_L^2}{2V.V_R}$
1.	200	190.5	60.644	0.606	36.781				
2.	210	200.0	63.673	0.636	40.582				
3.	220	209.5	66.70	0.667	44.55				

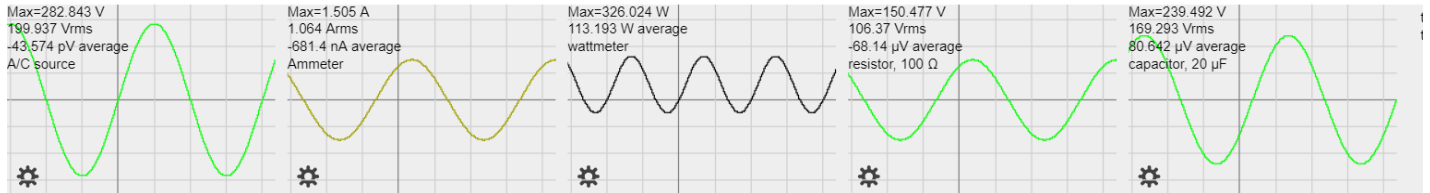
## Experiment 2(R-C Series Circuit) Falstad simulation readings



210V reading

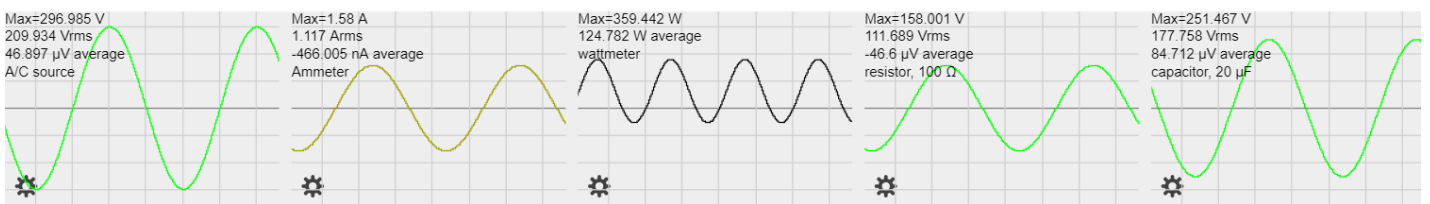

210 V reading

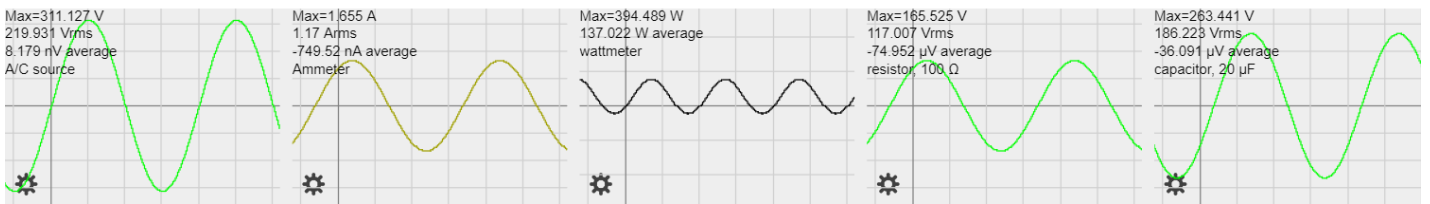


220V reading


**Calculations:-**

S. No.	Variac $V_s$	$V_C$	$V_R$	I	W	Calculated $V = \sqrt{V_C^2 + V_R^2}$	Power factor (Measured) $\cos \phi = \frac{W}{(V_s I)}$	Power factor (Measured 2) $\cos \phi = \cos[\tan^{-1}(\frac{V_C}{V_R})]$
1.	200	169.29	106.37	1.064	113.24			
2.	210	177.75	111.68	1.117	124.78			
3.	220	186.32	117.07	1.171	137.16			

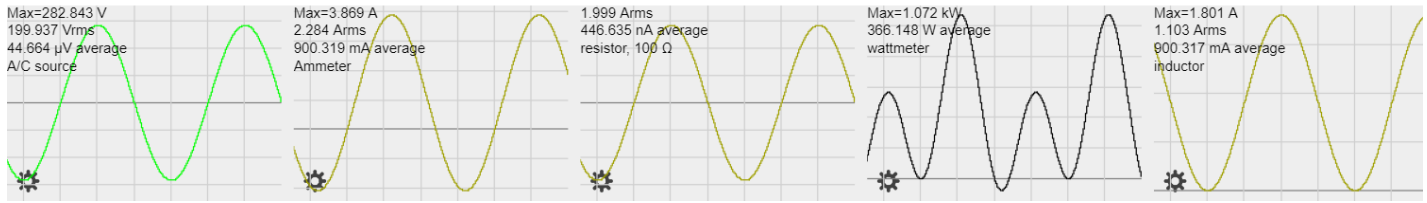
## Experiment 3 (R-L Parallel Circuit) Falstad simulation readings



200V

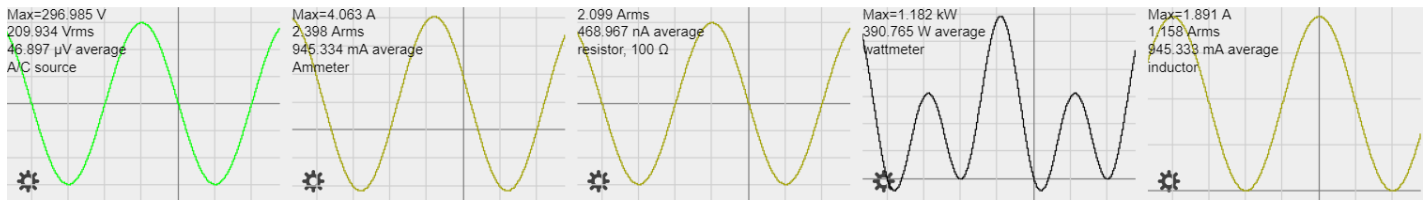

210 V

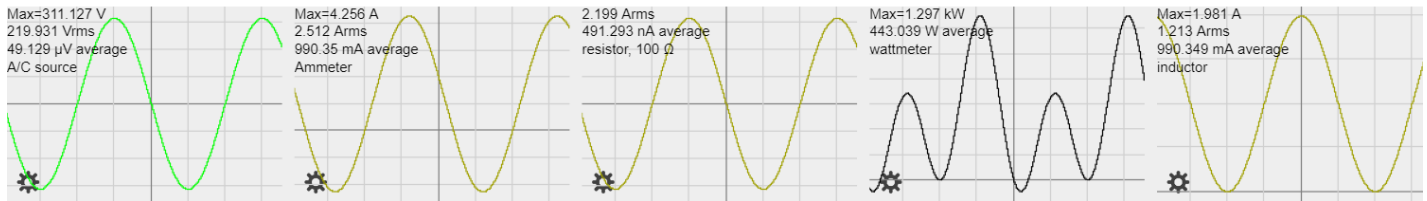


220 V


**Calculations:-**

S. No.	Variac $V_s$	I	$I_L$	$I_R$	W	Calculated $I = \sqrt{I_L^2 + I_R^2}$	Power factor (Measured) $\cos \phi = \frac{W}{(V_s I)}$	Power factor (Measured 2) $\cos \phi = \frac{I_R}{I}$
1.	200	2.284	1.103	1.999	372.84			
2.	210	2.398	1.158	2.099	411.05			
3.	220	2.512	1.213	2.199	451.13			

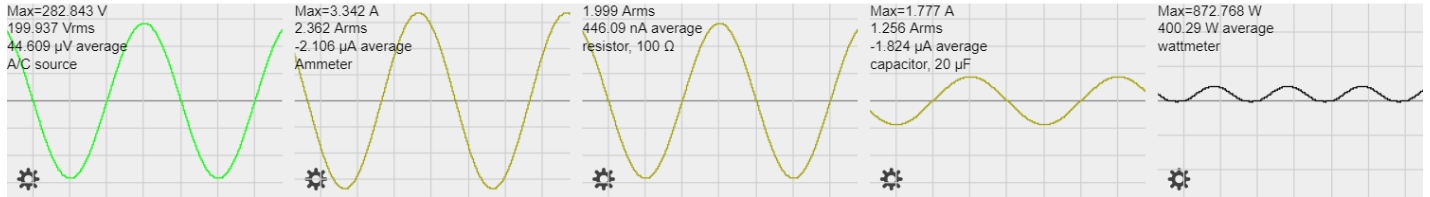
## Experiment 3 (R-C Parallel Circuit) Falstad simulation readings



200V

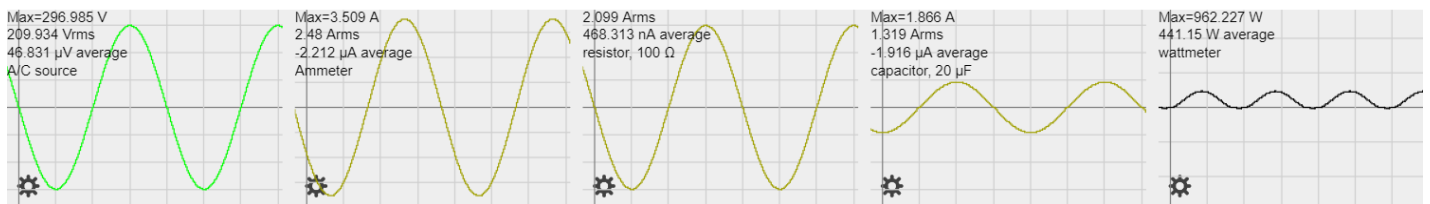

210V

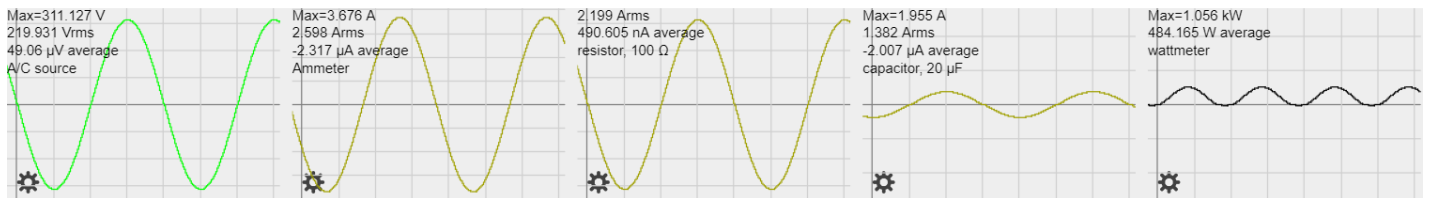

220V

**Calculations:-**



S. No.	Variac $V_s$	I	$I_c$	$I_R$	W	Calculated $I = \sqrt{I_c^2 + I_R^2}$	Power factor (Measured) $\cos \phi = \frac{W}{(V_s I)}$	Power factor (Measured 2) $\cos \phi = \frac{I_R}{I}$
1.	200	2.362	1.256	1.999	400.29			
2.	210	2.48	1.319	2.099	441.15			
3.	220	2.598	1.382	2.199	484.165			